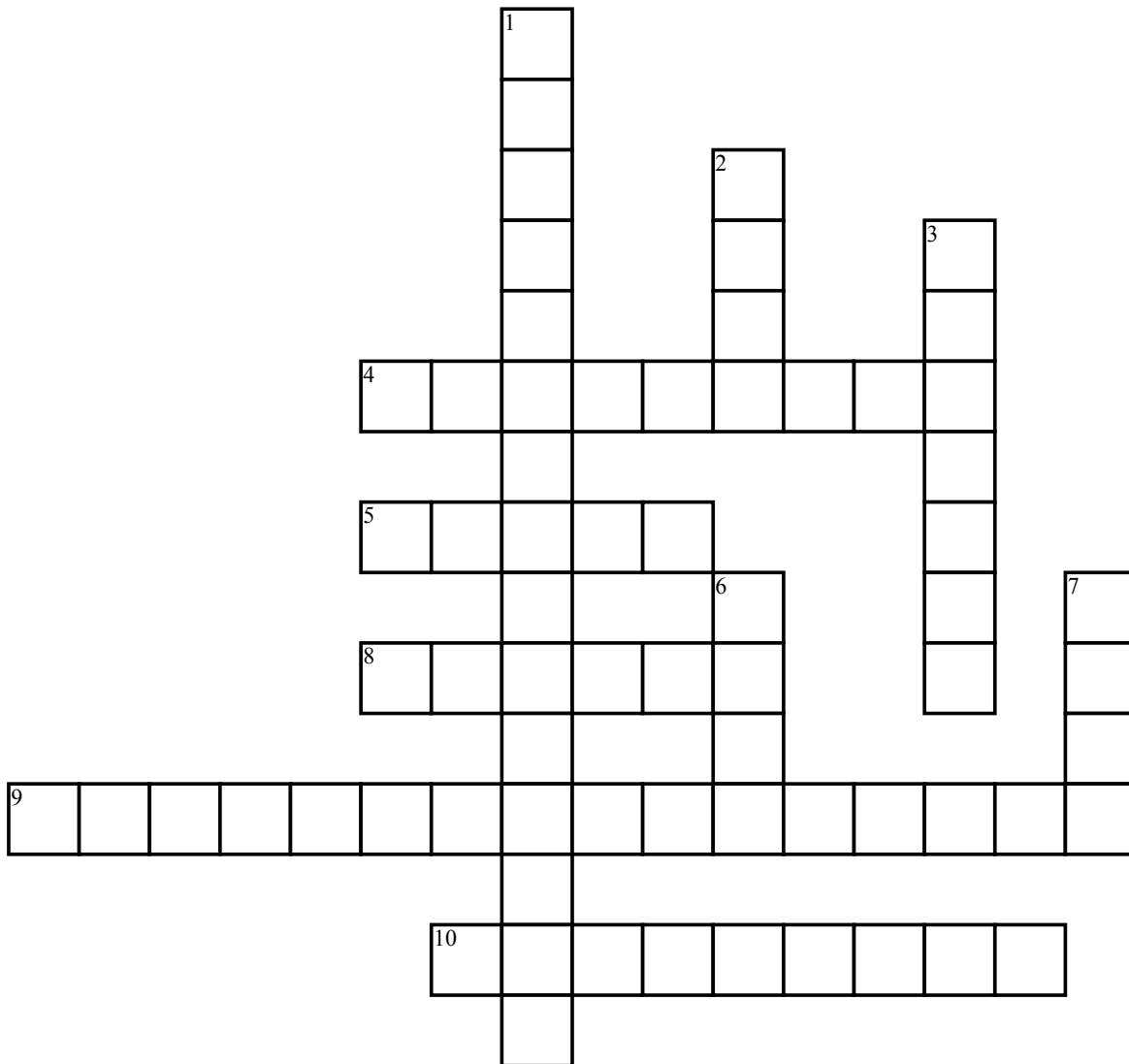


Electrical diagrams Crossword



Across

4. A device that is connected in parallel with the load
5. You should always use one when making a circuit diagram
8. Opens and closes the circuit
9. Powers the circuit
10. Converts electricity into light

Down

1. A circuit that divides the electrons
2. This item melts if the current gets too high
3. What does the ammeter measure
6. What is resistance measured in
7. Conductor; Allows electrons to flow