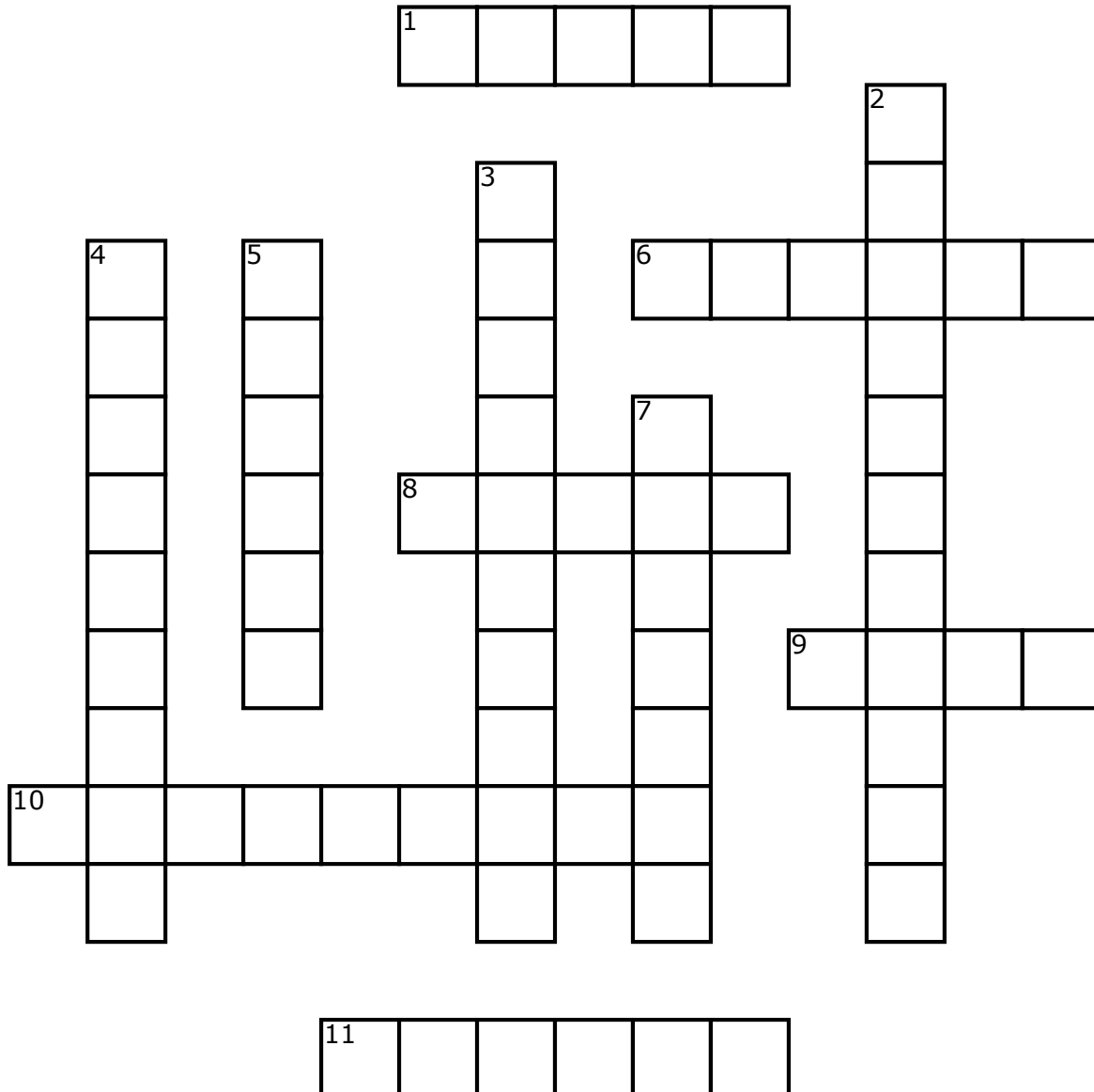


# Electricity



## **Across**

**1.** If an electrical item does not use a battery, you must plug it into the \_\_\_\_\_

**6.** for electricity to flow, a circuit must be \_\_\_\_\_

**8.** The name for energy we get from the sun \_\_\_\_\_

**9.** This will light up when the circuit is closed \_\_\_\_\_

**10.** This will allow electricity to flow through it \_\_\_\_\_

**11.** A component we use to turn circuits on and off \_\_\_\_\_

## **Down**

**2.** Non-renewable energy source from things that died millions of years ago \_\_\_\_\_

**3.** We learnt how to draw symbols for electronic \_\_\_\_\_

**4.** Something that won't conduct electricity \_\_\_\_\_

**5.** Makes a noise in a closed circuit \_\_\_\_\_

**7.** Multiple cells joined together \_\_\_\_\_