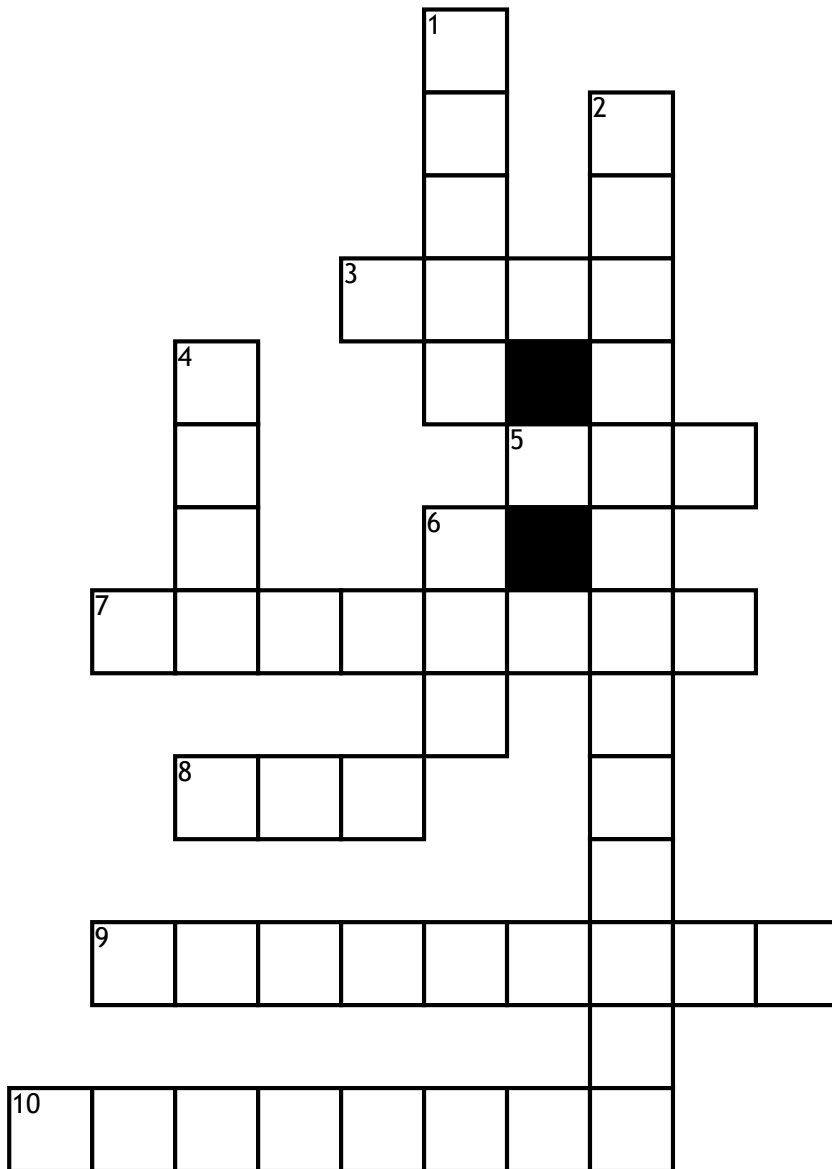


Tech puzzle



Across

3. what is the unit of power
5. How many bit flipflop stores?
7. What type of device consists of a coil with a moveable iron core?
8. The symbol is
9. The element that has biggest size in transistor?
10. JFET also called as _____ transistor?

Down

1. A capacitor and resistor connected in series is called _____ circuit?
2. A device used for dividing the voltage?
4. In open circuit, the current becomes _____?
6. The output will be a LOW for any case when one or more inputs are zero in _____ gate?